

**Programme: DT008 / 2**  
**ELEK2108 Electronics 1**  
**Laboratory Technical Report**

	Name	Student Number
<b>Author:</b>	<b>Talha Tallat</b>	<b>D18124645</b>
<b>Collaborator 1:</b>	-	-
<b>Collaborator 2:</b>	-	-
<b>Collaborator 3:</b>	-	-

<b>Laboratory Number:</b>	<b>D</b>
<b>Semester Week Number:</b>	<b>9</b>
<b>Date:</b>	<b>11/03/2019</b>

**Submission Checklist and Declaration**

To ensure that the focus of the assessment of your laboratory report can include the development of higher order skills and competences associated with a Level 7 qualification, please complete the checklist and declaration below.

**I declare that the report that I am submitting:**

- is my original work, with secondary sources acknowledged;
- was proofread thoroughly for typographical errors;
- contains citations with references formatted in the IEEE citation style.

I understand that my work can be returned uncorrected if the criteria are unfulfilled.

**Confirm**

- ☒
- ☒
- ☒

**Signature:**


*Talha*

## 1.0 Laboratory Aim

- Describe the purpose of the laboratory or the research.

The aim of this lab was to build a Cascaded 8 bit adder in Vivado.

 - Importing:
  - VHDL behavioural design source code
  - VHDL library source code
  - A VHDL simulation (Test bench) code to test the design
- Implement the design on the Artix-7 FPGA via the Basys3 development board
- Apply signals to the board switches to confirm that the design works as planned



## 2.0 Laboratory Procedure

- Describe the actions taken during the work.

The new project was created in the Vivado and was given a name and location. The Register Transfer level (RTL) was selected to be able to add source, run RTL analysis, synthesis and design planning and analysis.

The source files were added from the bright space 'ByteAdd.vhd' this file will be added/copied to the Byte\_Adder.xpr project that has just been created.

The Board was selected and library was added using "Add a design source" and the XSE.vhd was selected. The "testBench" simulation source file was added along with the ByteADD\_tb.vhd testbench.

The limit for the simulation runtime was set to 50ns and the behavioural simulation was run.

## 3.0 Results

- Present the results recorded from the investigation.

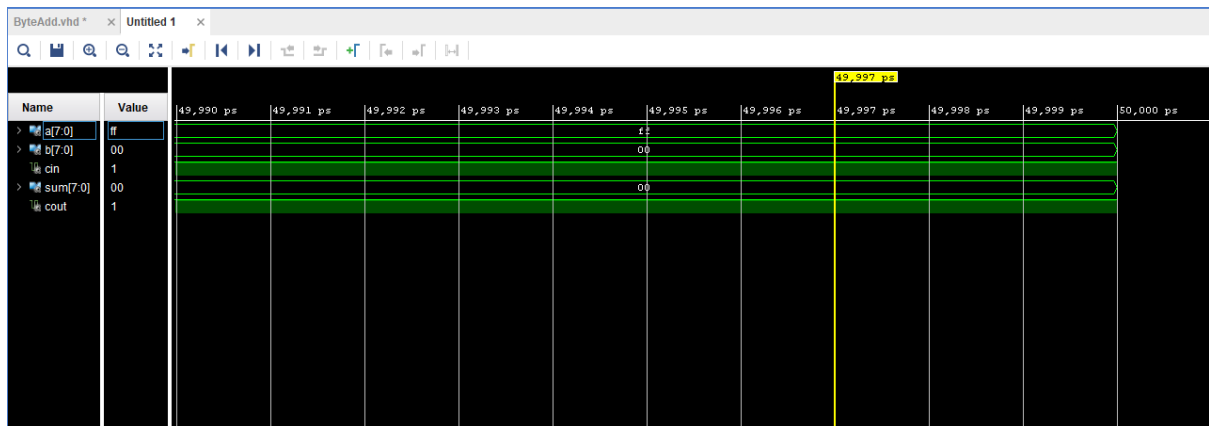


Figure 1 – Simulation Result

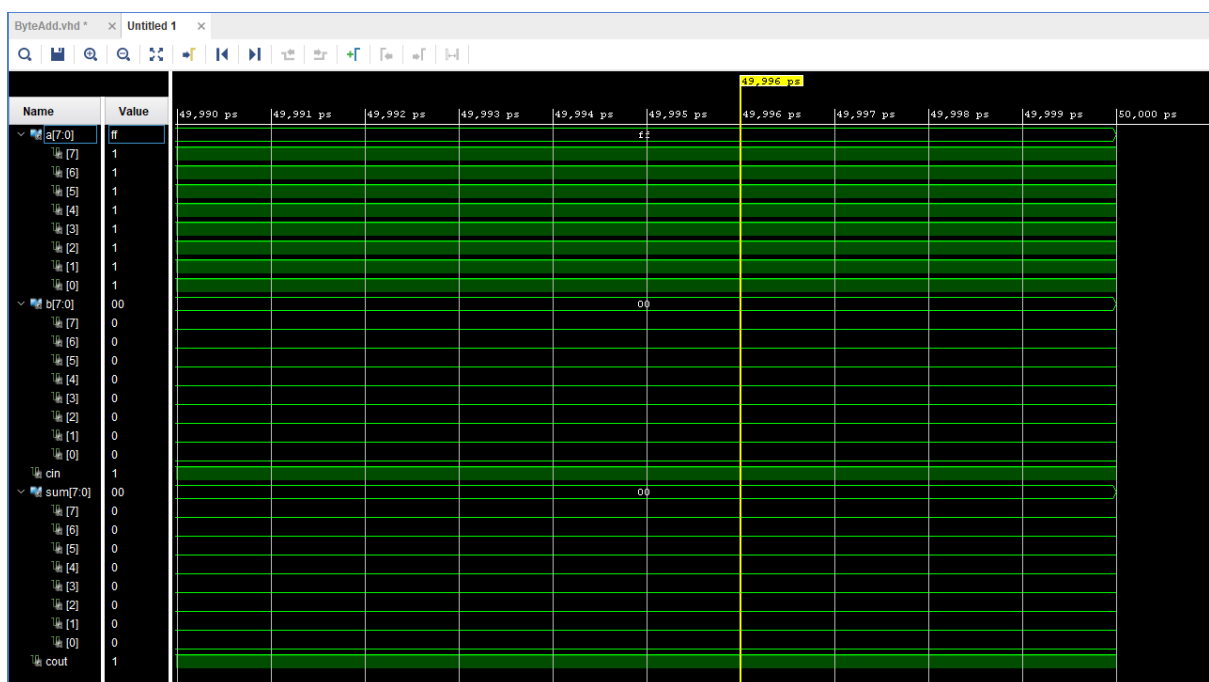


Figure 2 - Simulation Result

A	B	Cin	EXPECTED SUN (A+B)	EXPECTED Cout	Correct? t/f
00000000	00000000	0	00000000	0	t
00000100	00001100	0	00010000	0	t
11111111	00000000	1	00000000	1	t
01011110	11010101	0	00110011	1	t

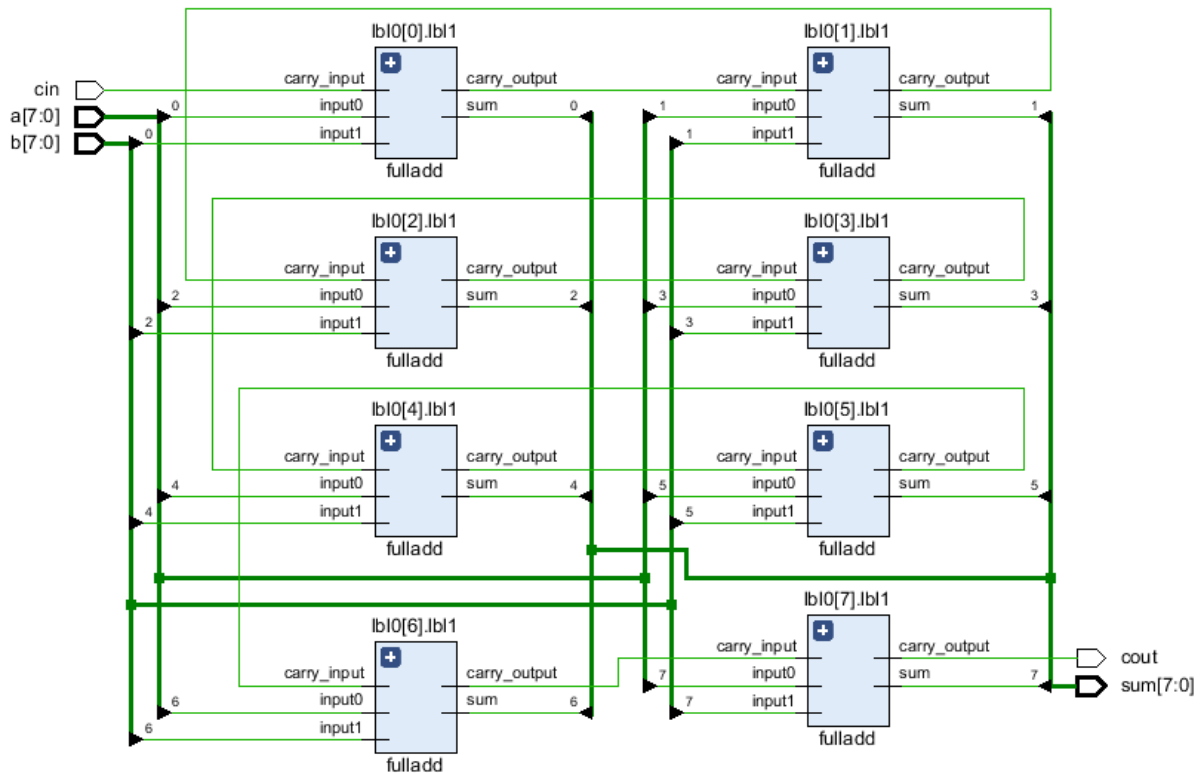


Figure 3 – Analysis Schematic diagram

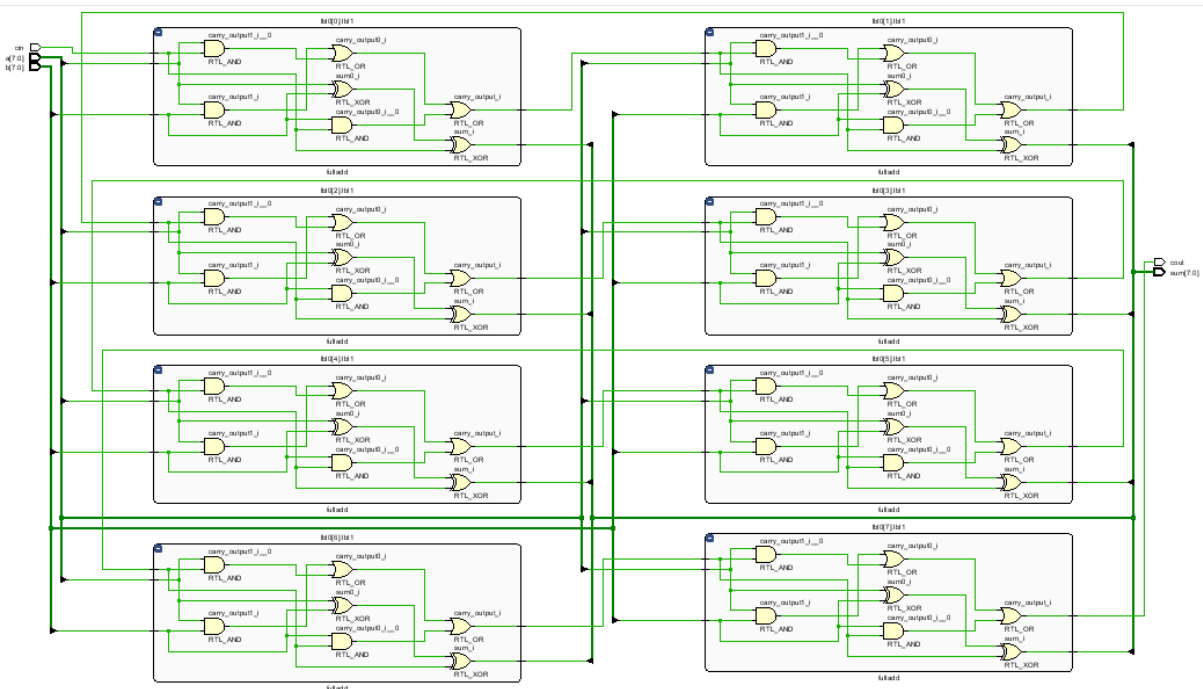


Figure 4 - Analysis Schematic diagram with logic gates



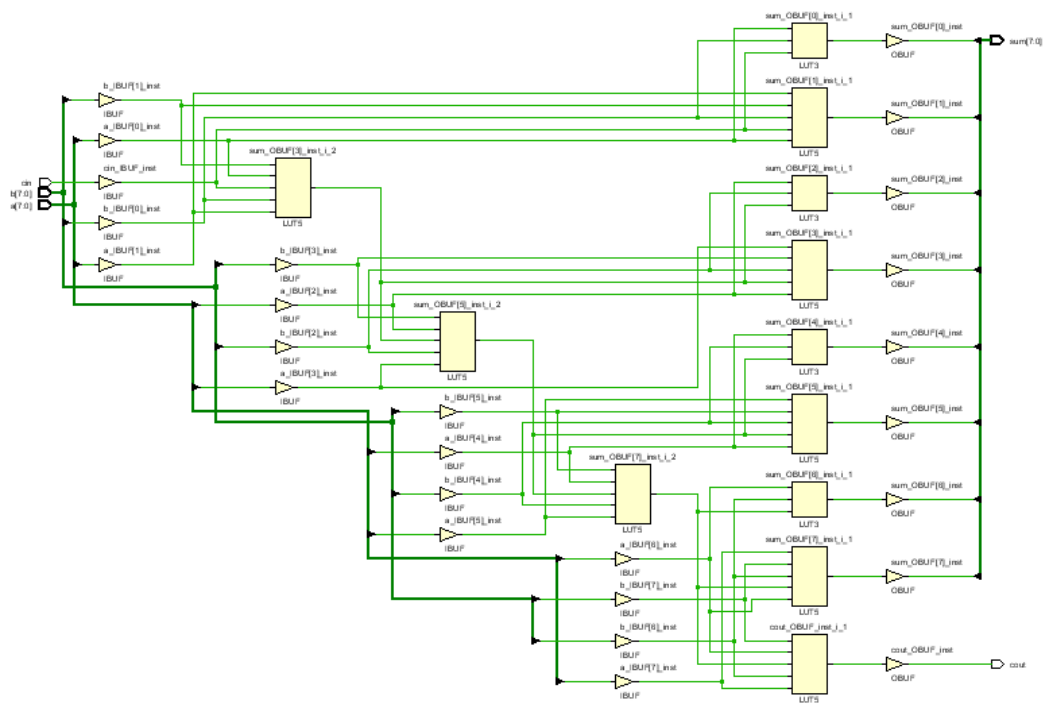




Figure 5 – Circuit diagram

 



Figure 6 – Elebart design

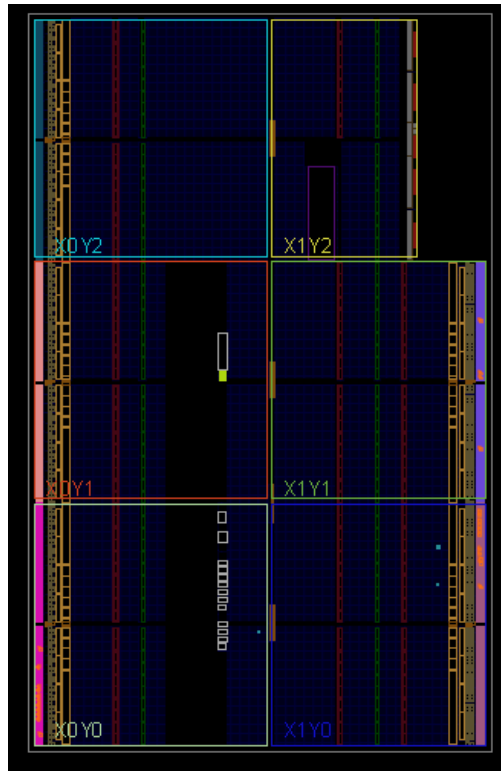



  



  

#### 4.0 Analysis

- Provide some comments that interpret what the results indicate or prove.

We saw two binary signals been inputted and we saw an output through the 8 bit adder.

#### 5.0 Conclusions



The things I have learned about the 8 bit adder that a full adder is made by combining two half-adders and an additional OR-gate. A full adder has the carry in capability and so allows cascading which results in the possibility of multi-bit addition. The circuit diagram for a full adder is given below, note that the two separate half-adders are each enclosed in a box to help understand this circuit.

## 6.0 References

<https://www.bing.com/images/search?view=detailV2&id=DE9F4FCD0B4FCEDC86C4FB25437AE82D6AAA34B5&thid=OIP.QmOoeHDXM80oGDBSGS0SHQHaEn&mediaurl=https%3A%2F%2Fi.pinimg.com%2F736x%2F4f%2F32%2F16%2F4f32169be852d0416cf4ff76068e6a06.jpg&exph=459&expw=736&q=8-Bit+Adder+Logic+Gates&selectedindex=3&ajaxhist=0&vt=0&eim=1,6>

### Submission Checklist

- |  |                                     |
|--|-------------------------------------|
| 1. The cover page is appropriately complete.                   | <input checked="" type="checkbox"/> |
| 2. The six sections in the body of the report are complete.    | <input checked="" type="checkbox"/> |
| 3. The constructive feedback from a collaborator is addressed. | <input checked="" type="checkbox"/> |
| 4. A final spell-check is completed.                           | <input checked="" type="checkbox"/> |
| 5. A backup copy of the report is online.                      | <input checked="" type="checkbox"/> |